

5 Computer Architecture¹

This chapter is the pinnacle of the hardware part of our journey. We are now ready to take all the chips that we’ve built in chapters 1–3 and integrate them into a general-purpose computer system capable of running programs written in the machine language presented in chapter 4. The specific computer we will build, called *Hack*, has two important virtues. On the one hand, Hack is a simple machine that can be constructed in just a few hours, using previously built chips and the hardware simulator supplied with the book. On the other hand, Hack is sufficiently powerful to illustrate the key operating principles and hardware elements of any general-purpose computer. Therefore, building it will give you an excellent understanding of how modern computers work at the low hardware and software levels.

Section 5.1 begins with an overview of the *von Neumann architecture* — a central dogma in computer science underlying the design of almost all modern computers. The Hack platform is a von Neumann machine variant, and section 5.2 gives its exact hardware specification. Section 5.3 describes how the Hack platform can be implemented from previously built chips, in particular the ALU built in project 2 and the registers and memory systems built in project 3. Section 5.4 compares the Hack machine with industrial-strength computers, and emphasizes the critical role that optimization plays in the latter. Section 5.5 gives an overview of the computer construction project.

The computer that will emerge from this project will be as simple as possible, but not simpler. On the one hand, the computer will be based on a minimal and compact hardware configuration. On the other hand, this configuration will be sufficiently powerful for executing programs written in a Java-like programming language, delivering a reasonable performance and a satisfying user experience.

¹ Chapter 5 from *The Elements of Computing Systems* by Noam Nisan and Shimon Schocken, Second Edition, MIT Press, forthcoming 2017.

5.1 Computer Architecture Fundamentals

5.1.1 The Stored Program Concept

Compared to all the other machines around us, the most unique feature of the digital computer is its amazing versatility. Here is a machine with finite hardware that can perform an infinite number of tasks, from playing games to publishing books to designing airplanes. This remarkable versatility—a boon that we have come to take for granted—is the fruit of a brilliant idea called the *stored program* concept. Formulated independently by several scientists and engineers in the 1930s, the stored program concept is still considered the most profound invention in, if not the very foundation of, modern computer science.

Like many scientific breakthroughs, the basic idea is remarkably simple. The computer is based on a fixed hardware platform, capable of executing a fixed repertoire of very simple instructions. At the same time, these instructions can be combined like building blocks, yielding arbitrarily sophisticated programs. Moreover, the logic of these programs is not embedded in the hardware, as it was in mechanical computers predating 1930. Instead, the program’s code is temporarily stored and manipulated in the computer’s memory, *just like data*, becoming what is known as “software.” Since the computer’s operation manifests itself to the user through the currently executing software, the same hardware platform can be made to behave completely differently each time it is loaded with a different program.

5.1.2 The von Neumann Architecture

The stored program concept is a key element of many abstract and practical computer models, most notably the *universal Turing machine* (1936) and the *von Neumann machine* (1945). The Turing machine—an abstract artifact describing a deceptively simple computer—is used mainly in theoretical computer science, for analyzing the logical foundations of computational

problems and solutions. In contrast, the von Neumann machine is a practical architecture and the conceptual blueprint of almost all computer platforms today.

The von Neumann architecture, shown in diagram 5.1, is based on a *central processing unit* (CPU), interacting with a *memory* device, receiving data from some *input* device, and sending data to some *output* device. At the heart of this architecture lies the *stored program* concept: The computer's memory stores not only the data that the computer manipulates, but also the very instructions that tell the computer what to do. Let us explore this architecture in some detail.

 


Diagram 5.1: the von Neumann architecture

5.1.3 Memory

Like other hardware elements, the memory unit can be discussed from a physical perspective and from a logical perspective. Physically, the memory is a linear sequence of addressable *registers*, each having a unique address and a value, which is a fixed-size word of information. Logically, the memory is divided into two areas. One area is dedicated for storing data, e.g. the arrays and objects of programs that are presently executing, while the other area is dedicated for storing the programs' instructions. Although all these “data words” and “instruction words” look exactly the same physically, they serve very different purposes.

In some von Neumann architecture variants, the data memory and the instruction memory are managed within the same physical memory unit, as was just explained. In other variants, the data memory and the instruction memory are kept in separate physical memory units that have distinct address spaces. This setting, sometimes referred to as “Harvard architecture”, is also the architecture of our Hack computer. Both variants have certain advantages that will be discussed later in the chapter.

All the memory registers—irrespective of their roles—are accessed in the same way: in order to manipulate a particular memory register, one must first select the register by supplying an address. This action provides an immediate access to the register's data. The term *Random Access Memory* (RAM) is often used to denote the important fact that each randomly selected register can be reached in the same access time, irrespective of the memory size and the register's location in it.

Data Memory: High-level programs manipulate abstract artifacts like variables, arrays, and objects. After the programs are translated into machine language, these data abstractions become binary codes, stored in the computer's memory. Once an individual register has been

selected from the memory by specifying its address, its contents can be either *read* or *written* to. In the former case, we retrieve the value of the selected register. In the latter case, we store a new value in the selected register, overriding the previous value. Such memories are sometimes referred to as “read/write” memories.

Instruction Memory: Before high-level programs can be executed on the computer, they must be translated into machine language. Following this translation, each high-level statement becomes a series of one or more machine language instructions. These instructions are stored in the computer’s *instruction memory* as binary codes. In each step of a program’s execution, the CPU *fetches* (i.e., *reads*) a binary machine instruction from a selected register in the instruction memory, decodes it, executes the specified instruction, and figures out which instruction to fetch and execute next.

We see that before executing a particular program, we must first load the program’s code into the instruction memory, typically from some peripheral mass storage device like a disk. Given the compact and highly focused perspective of a von Neumann machine, *how* a program is loaded into the computer’s instruction memory is considered an external issue. What’s important is that when the CPU is called upon to execute a program, the program’s code will already reside in memory, one way or another. As you saw in chapter 4, the act of loading a program into the instruction memory from an external text file is supported by the supplied CPU emulator.

5.1.4 Central Processing Unit

The CPU—the centerpiece of the computer’s architecture—is in charge of executing the instructions of the currently loaded program. These instructions tell the CPU which calculation it has to perform, which registers it has to read from or write to, and which instruction it has to fetch and execute next. The CPU executes these tasks using three main hardware elements: an *Arithmetic-Logic Unit* (ALU), a set of *registers*, and a *control unit*.

Arithmetic Logic Unit: The ALU chip is built to perform all the low-level arithmetic and logical operations featured by the computer. For example, a typical ALU can add two numbers, compute a bitwise And function on two numbers, compare two numbers, and so on. How much functionality an ALU should have is a matter of need, budget, energy, and similar cost-effectiveness considerations. Any function not supported by the ALU as a primitive hardware operation can be later realized by the computer's system software (yielding a slower implementation, of course).

Registers: Since the CPU is the computer's centerpiece, it must perform as efficiently as possible. In order to boost performance, it is desirable to store the intermediate results that computer programs generate locally, close to the ALU, rather than ship them in and out of the CPU chip and store them in some remote and separate RAM chip. Thus, a CPU is typically equipped with a small set of 2 up to 32 resident high-speed *registers*, each capable of holding a single word.

Control Unit: A computer instruction is represented as a binary code, typically 16, 32, or 64 bits wide. Before such an instruction can be executed, it must be decoded, and the information embedded in it must be used to signal various hardware devices (ALU, registers, memory) how to execute the instruction. The instruction decoding is done by some *control unit*, which is also responsible for figuring out which instruction to fetch and execute next.

The CPU operation can now be described as a repeated loop: decode the current instruction, execute it, figure out which instruction to execute next, fetch it, decode it, and so on. This process is sometimes referred to as the “fetch-execute cycle”.

5.1.5 Registers

When talking about computer hardware, the term “register” is used quite liberally to refer to any device capable of storing a chunk of bits that represents some stand-alone value like a variable

value, an instruction, or an address. According to this broad definition, any memory location is in fact a register, and so of course are the registers that reside inside the CPU. This section is dedicated to a discussion of these CPU-resident registers.

Suppose we didn't have any CPU-resident registers. This would imply that any CPU operation that requires inputs or outputs would have to rely on memory access. Let us consider what each such memory access entails. First, some address value travels from the CPU to the RAM's address input. Next, the RAM's direct-access logic uses the supplied address to select a specific memory register. Finally, the register's contents either travels back to the CPU (a read operation), or is replaced by some additional value that travels from the CPU (a write operation).

Note that this elaborate process involves at least two separate chips, an address bus, and a data bus, resulting in an expensive and time-consuming operation. This stands in sharp contrast to the ALU, which is a lean and mean combinational machine. Thus we have a lightning fast calculator that depends on a sluggish data store for supplying inputs and consuming outputs. The result may well lead to what is sometimes called *starvation*, which is what happens when a processor is denied the resources it needs to complete its work.

Clearly, if we could have placed a few high-speed registers inside the CPU itself, right next to the ALU, we could have saved ourselves a great deal of time and overhead. There is another, subtle but critically important advantage for using CPU-resident registers. In order to specify an instruction that includes a memory register, like `Memory[addr]=value`, we must supply a memory address, which typically requires many bits. In the 16-bit Hack platform, this technical detail alone forces us to use *two* machine instructions, and *two* clock cycles, even for performing mundane tasks like `Memory[addr]=0` or `Memory[addr]=1`.

In contrast, since there are normally only a few CPU-resident registers, identifying each one of them requires only a few bits. Therefore, an operation like `someCPURegister=0` or

someCPURegister=1 requires only one machine instruction, and one cycle. To sum up, CPU-resident registers save unnecessary memory access, and allow using thinner instruction formats, resulting in faster throughput. The remainder of this section describes the registers that CPU's typically use.

Data registers: These registers give the CPU short-term memory services. For example, if a program wants to calculate $(a - b) \cdot c$, we must first compute and remember the value of $(a - b)$. In principle, this temporary result can be stored in some memory register. Clearly, a much more sensible solution is to store it locally inside the CPU, using a *data register*. Typically, CPU's use at least one and up to 32 data registers.

Address registers: Many machine language instructions involve memory access: reading data, writing data, and fetching instructions. In any one of these operations, we must specify which memory register we wish to operate on. This is done by supplying an address. In some cases, the address is coded as part of the instruction, while in other cases the address is specified, or computed, by some previous instruction. In the latter case, the address must be stored somewhere. This is done using a CPU-resident chip called *address register*.

Unlike regular registers, the output of an address register is typically connected to the address input of a memory device. Therefore, placing a value in the address register has the side effect of selecting a particular memory register, and this register makes itself available to subsequent instructions designed to manipulate it. For example, suppose we wish to set `Memory[17]` to 1. In the Hack language, this can be done using the pair of instructions `@17` (which sets `A=17` and makes the `M` mnemonic stand for `Memory[17]`), followed by `M=1` (which sets the selected memory register to 1).

In addition to supporting this fundamental addressing operation, an address register is, well, a register. Therefore, if needed, it can be used as yet another data register. For example,

suppose we wish to set the D register to 17. This can be done using the pair of instructions @17, followed by D=A. Here we use A not as an address register, but rather as a data register. The fact that Memory[17] was selected as a side effect of @17 is completely ignored.

Program counter: When executing a program, the CPU must always keep track of the address of the instruction that must be fetched and executed next. This address is kept in a special register called *program counter*, or PC. The contents of the PC is computed and updated as a side effect of executing the current instruction, as we elaborate later in the chapter.

5.1.6 Input and Output

Computers interact with their external environments using a diverse array of input and output (I/O) devices. These include screens, keyboards, disks, printers, scanners, network interface cards, and so on, not to mention the bewildering array of proprietary components that embedded computers are called to control in automobiles, cameras, medical devices, and so on. There are two reasons why we don't concern ourselves here with the low-level architecture of these various devices. First, every one of them represents a unique piece of machinery requiring a unique knowledge of engineering. Second, and for this very same reason, computer scientists have devised clever schemes to make all these different devices look exactly the same to the computer. The key trick in managing this complexity is called *memory-mapped I/O*.

The basic idea is to create a binary emulation of the I/O device, making it “look” to the CPU as if it were a regular memory segment. In particular, each I/O device is allocated an exclusive area in memory, becoming its “memory map.” In the case of an input device like a keyboard, the memory map is made to continuously reflect the physical state of the device: when the user presses a key on the keyboard, a binary code representing that key appears in the keyboard's memory map. In the case of an output device like a screen, the screen is made to continuously reflect the state of its designated memory map: when we write a bit in the screen's

memory map, a certain pixel turns on or off on the screen. The I/O devices are “refreshed” from the memory (and vice versa) several times per second, so the response time from the user’s perspective is almost instantaneous. Programmatically, the key implication is that computer programs can access any I/O device by simply manipulating selected registers in their designated memory areas.

Obviously, this arrangement is based on several agreed-upon contracts. First, the data that drives each I/O device must be serialized, or “mapped”, on the computer’s memory, hence the name “memory map”. For example, the screen, which can be viewed as a 2-dimensional grid of pixels, must be mapped on a 1-dimensional vector of fixed-size memory registers. Second, each I/O device is required to support some agreed-upon interaction protocol, so that programs will be able to access it in a predictable manner. For example, it should be decided, and agreed-upon, which binary codes should represent which keys on the keyboard. As a side comment, given the multitude of computer platforms, I/O devices, and different hardware and software vendors, one can appreciate the crucial role that *standards* play in determining these low-level interaction contracts.

The practical implications of a memory-mapped I/O architecture are significant: The design of the CPU and the overall platform can be totally independent of the number, nature, or make of the I/O devices that interact, or will interact, with the computer. Whenever we want to connect a new I/O device to the computer, all we have to do is allocate to it a new memory map and “take note” of its base address (these one-time configurations are typically done by the operating system). From this point onward, any program that wants to manipulate this I/O device can do so—all it needs to do is manipulate selected registers in the memory map designated to represent the device.

The architectural framework described thus far in the chapter is characteristic of any general-purpose computer system. We now turn to describe one specific example of this architecture: the Hack computer.

5.2 The Hack Hardware Platform: Specification

5.2.1 Overview

The Hack platform is a 16-bit von Neumann machine, designed to execute programs written in the Hack machine language presented in chapter 4. In order to do so, the Hack platform consists of a *CPU*, two separate memory modules serving as *instruction memory* and *data memory*, and two memory-mapped I/O devices: a *screen* and a *keyboard*.

The Hack computer executes programs that reside in an instruction memory. In physical implementations of the Hack platform, this memory can be implemented using a ROM chip that is pre-loaded with the required program. Software-based simulators of the Hack computer are expected to support this functionality by providing means for loading the instruction memory from a text file containing a program written in the Hack machine language.

The Hack CPU consists of the ALU built in project 2 and three registers called *data register* (D), *address register* (A), and *program counter* (PC), identical to the 16-bit registers built in project 3. While the D-register is used solely for storing data values, the A-register serves three different purposes, depending on the context in which it is used: storing a data value (just like the D-register), pointing at an address in the instruction memory, or pointing at an address in the data memory. More about this, later.

The Hack CPU is designed to execute instructions written in the Hack machine language. These instructions have the 16-bit format “*ixxacccccddjjj*”. The *i*-bit (also known as *opcode*) codes the instruction *type*, which is either 0 for an *A*-instruction or 1 for a *C*-instruction. In case of an *A*-instruction, the instruction is treated as a 16-bit binary value which is loaded

into the A register. In case of a *C*-instruction, the instruction is treated as a sequence of control bits that determine which function the ALU should compute, and in which registers the computed value should be stored. In the course of executing any one of these instructions, the CPU also figures out which instruction in the program should be fetched and executed next.

We now turn to specify the various components of the Hack hardware platform.

5.2.2 Central Processing Unit (CPU)

The CPU of the Hack platform is designed to execute 16-bit instructions according to the Hack machine language specification presented in chapter 4. The Hack CPU expects to be connected to two separate memory modules: an instruction memory, from which it fetches instructions for execution, and a data memory, from which it can read, and into which it can write, data values. Diagram 5.2 gives the complete CPU specification.


5.2.3 Instruction Memory

The Hack *instruction memory* is implemented in a direct-access *Read-Only Memory* device, also called ROM. The Hack ROM consists of 32K addressable 16-bit registers, as shown in diagram 5.3.

 5.2.4 Input / Output

Access to the input/output devices of the Hack computer is made possible by the computer's *data memory*, a read-write RAM device consisting of 32K addressable 16-bit registers. In addition to serving as the computer's general-purpose data store, the data memory also interfaces between the CPU and the computer's input/output devices, as we now turn to specify.

In order to facilitate interaction with a user, the Hack platform can be connected to two peripheral devices: a *screen* and a *keyboard*. Both devices interact with the computer platform through *memory-mapped* buffers. Specifically, screen images can be drawn and probed by



/** The Hack Central Processing Unit consists of an ALU, two registers named A and D, and a program counter named PC (these internal chip-parts are not shown in the diagram). The `inM` input and `outM` output hold the values referred to as “M” in the Hack instruction syntax. The `addressM` output holds the memory address to which `outM` should be written.

The CPU is designed to fetch and execute instructions written in the Hack machine language. If `instruction` is an A-instruction, the CPU loads the 16-bit constant that the instruction represents into the A register. If `instruction` is a C-instruction, then (i) the CPU causes the ALU to perform the computation specified by the instruction, and (ii) the CPU causes this value to be stored in the subset of {A,D,M} registers specified by the instruction. If one of these registers is M, the CPU asserts the `writeM` control bit output (when `writeM` is 0, any value may appear in `outM`).

When the `reset` input is 0, the CPU uses the ALU output and the jump directive specified by the instruction to compute the address of the next instruction, and emits this address to the `pc` output. If the `reset` input is 1, the CPU sets `pc` to 0.

The `outM` and `writeM` outputs are *combinational*, and are affected instantaneously by the instruction’s execution. The `addressM` and `pc` outputs are *clocked*: although they are affected by the instruction’s execution, they commit to their new values only in the next time step. */

CHIP CPU

IN

```
instruction[16], // Instruction to execute.
inM[16],        // Value of Mem[A], the instruction’s M input
reset;          // Signals whether to continue executing the current program
                // (reset==1) or restart the current program (reset==0).
```


OUT

```
outM[16],       // Value to write to Mem[addressM], the instruction’s M output
addressM[15],   // In which address to write?
writeM,         // Write to the Memory?
pc[15];         // address of next instruction
```

Diagram 5.2: The Hack Central Processing Unit (CPU) interface

writing and reading, respectively, 16-bit values in a designated memory segment called *screen memory map*. Similarly, which key is presently pressed on the keyboard can be determined by probing a designated memory register called *keyboard memory map*.

 The memory maps interact with their respective I/O devices via peripheral logic that resides outside the computer. The contract is as follows: When a bit is changed in the screen's memory map, a respective black and white pixel is drawn on the physical screen. When a key is pressed on the physical keyboard, the respective scan-code of this key appears in the keyboard's memory map.



```
/** The instruction memory of the Hack computer, implemented as a  
read-only memory of 32K registers, each 16-bit wide.
```

```
Performs the operation out = ROM32K[address].
```

```
In words: outputs the 16-bit value stored in the register selected by the  
address input. This value is taken to be the current instruction.
```

```
It is assumed that the chip is preloaded with a program written in the  
Hack machine language.
```

```
Software-based simulators of the Hack computer are expected to  
provide means for loading the chip with a Hack program, either  
interactively, or using a test script. */
```

```
CHIP ROM32K
```

```
IN address[15];
```

```
OUT out[16];
```

Diagram 5.3: The Hack Instruction Memory interface.

We now turn to specifying the built-in chips that interface between the hardware platform and the I/O devices. This will set the stage for specifying the complete memory module that embeds these chips.

Screen: The Hack computer can interact with a physical screen consisting of 256 rows of 512 black-and-white pixels each. The computer interfaces with the physical screen via a memory map, implemented by a RAM chip called **Screen**. This chip behaves like regular memory, meaning that it can be read and written to. In addition, it features the side effect that any bit written to it is reflected as a pixel on the physical screen (1 = black, 0 = white). The exact mapping between the memory map and the physical screen is specified in diagram 5.4.

```
/** The Screen (memory map) functions exactly like a 16-bit, 8K RAM:
```

```
(1) out(t) = Screen[address(t)](t)
```

```
(2) if load(t) then Screen[address(t)](t+1) = in(t)
```

The chip implementation has the side effect of continuously refreshing a physical screen. The physical screen consists of 256 rows and 512 columns of black and white pixels (simulators of the Hack computer are expected to simulate this screen).

Each row in the physical screen, starting at the top left corner, is represented in the **Screen** memory map by 32 consecutive 16-bit words. Thus the pixel at row r from the top and column c from the left ($0 \leq r \leq 255$, $0 \leq c \leq 511$) is mapped on the $c\%16$ bit (counting from LSB to MSB) of the 16-bit word stored in **Screen** $[r * 32 + c / 16]$. */

```
CHIP Screen
```

```
IN
```

```
    in[16],          // what to write
    address[13];     // where to write (or read)
    load,            // write-enable bit
```

```
OUT
```

```
    out[16];         // Screen value at the given address
```

Diagram 5.4: The Hack Screen chip interface

Keyboard: The Hack computer can interact with a physical keyboard, like that of a personal computer. The computer interfaces with the physical keyboard via a chip called `Keyboard`. When a key is pressed on the physical keyboard, a unique 16-bit scan-code is emitted to the output of the `Keyboard` chip. When no key is pressed, the chip outputs `0`. The character set of the Hack platform is given in Appendix C, along with the scan-code of each character.

```
/** The Keyboard (memory map) is connected to a standard, physical
keyboard. It is made to output the 16-bit scan-code associated with the
key which is presently pressed on the physical keyboard, or 0 if no key is
pressed.

The keyboard scan-codes are given in Appendix C of the book.
Simulators of the Hack computer are expected to implement the contract
described above. */


CHIP Keyboard

OUT out[16];    // The scan-code of the pressed key,
                // or 0 if no key is currently pressed.
```

Diagram 5.5: The Hack Keyboard chip interface

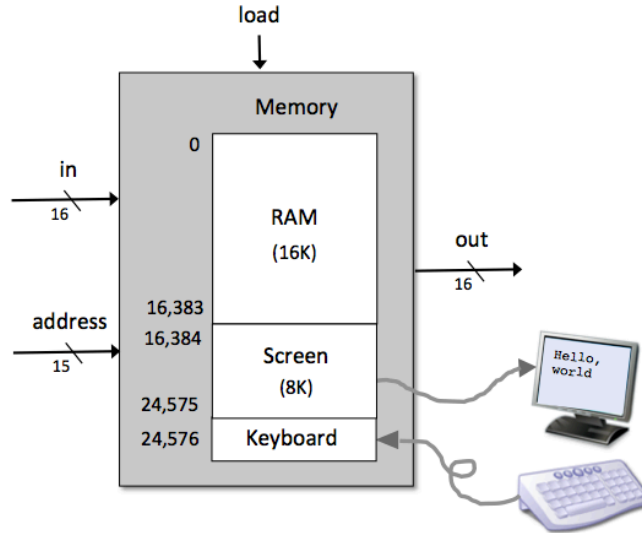5.2.6 Data Memory

The overall address space known as the Hack *data memory* is realized by a chip called `Memory`. This chip is essentially a package of three 16-bit storage devices: a RAM (16K registers, for regular data storage), a `Screen` (8K registers, acting as the screen memory map), and a `Keyboard` (1 register, acting as the keyboard memory map). The complete specification is given in diagram 5.6.



/** The complete address space of the Hack computer's data memory, including RAM and memory-mapped I/O. Facilitates read and write operations, as follows:

Read: $\text{out}(t) = \text{Mem}[\text{address}(t)](t)$

Write: $\text{if load}(t) \text{ then Mem}[\text{address}(t)](t+1) = \text{in}(t)$

In words: the chip always outputs the value stored at the memory location specified by **address**.

If $\text{load}==1$, the **in** value is loaded into the register specified by **address**. This value becomes available through the **out** output from the next time step onward.

The memory access rules are as follows:

Only the top $16K+8K+1$ words of the address space are used.

$0x0000-0x5FFF$: accessing an address in this range results in accessing the RAM.

$0x4000-0x5FFF$: accessing an address in this range results in accessing the Screen.

$0x6000$: accessing this address results in accessing the Keyboard.

$> 0x6000$: accessing an address in this range is invalid. */

CHIP Memory


IN $\text{in}[16]$, load , $\text{address}[15]$;

OUT $\text{out}[16]$;

Diagram 5.6: The Hack Data Memory interface

 5.2.7 Computer

The topmost chip in the Hack hardware hierarchy is a Computer chip consisting of a CPU, an instruction memory, and a data memory. The computer can interact with a screen and a keyboard. The complete specification is given in diagram 5.7.



```
/** The HACK computer, consisting of CPU, ROM and Memory parts
    (these internal chip-parts are not shown in the diagram).
    When reset==0, the program stored in the computer's ROM executes.
    When reset==1, the execution of the program restarts.
    Thus, to start a program's execution, the reset input must be pushed "up"
    (signaling 1) and "down" (signaling 0).
    From this point onward, the user is at the mercy of the software. In
    particular, depending on the program's code, the screen may show some
    output, and the user may be able to interact with the computer via the
    keyboard. */

CHIP Computer
IN    reset;
```

Diagram 5.7: Interface of the topmost chip in the Hack hardware platform, named Computer.

5.3 Implementation

This section outlines how a hardware platform can be built to realize the Hack computer specification described in the previous section. As usual, we don't give exact building instructions. Rather, we expect readers to discover and complete the implementation details on their own. All the chips described below can be built in HDL and simulated on a personal computer, using the hardware simulator supplied with the book. As usual, technical details are given in the final Project section of this chapter.

5.3.1 The Central Processing Unit

When we set out to implement the Hack CPU, our objective is to come up with a logic gate architecture capable of (i) executing a given Hack instruction, and (ii) determining which instruction should be fetched and executed next. In order to do so, the proposed CPU implementation includes an ALU chip capable of computing arithmetic/logical functions, a set of registers, a program counter, and some additional gates designed to help decode, execute, and fetch instructions. Since all these building blocks were already built in previous chapters, the key question that we face now is how to arrange and connect them in a way that effects the desired CPU operation. One possible configuration is illustrated in diagram 5.8.

The architecture shown in diagram 5.8 is used to perform three classical CPU tasks: decoding the current instruction, executing the current instruction, and deciding which instruction to fetch and execute next. We now turn to describe these three tasks.

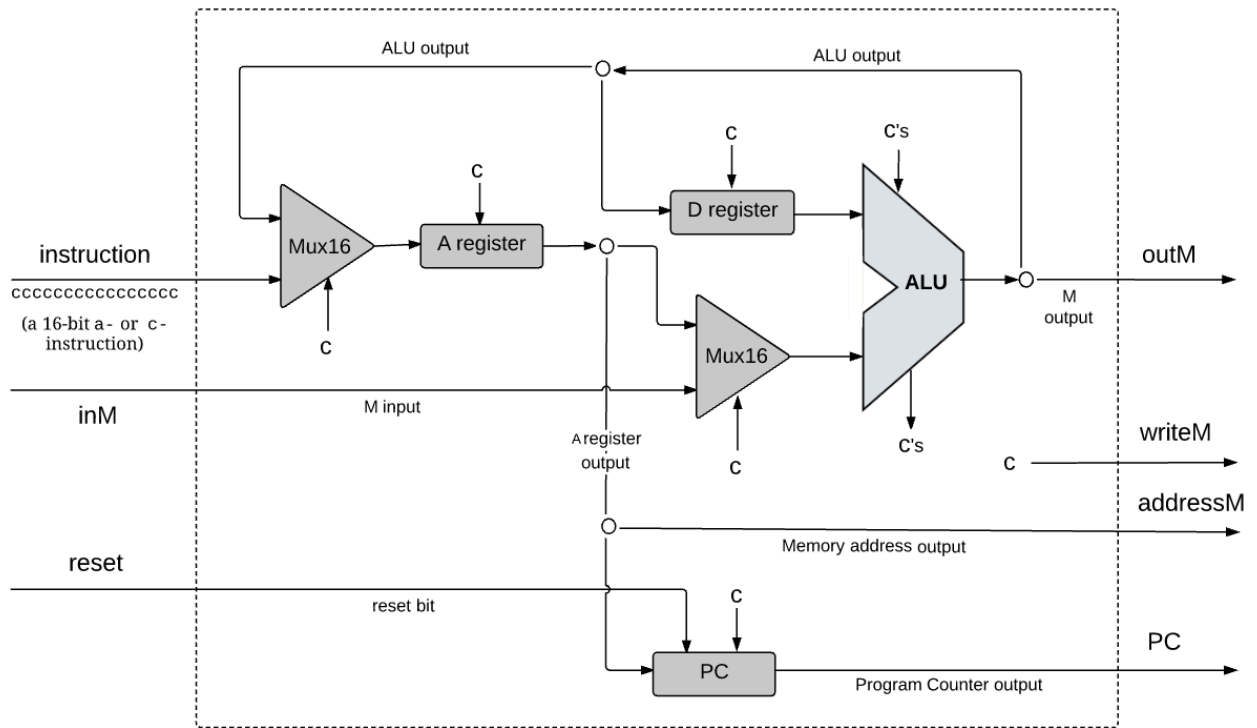


Diagram 5.8: Proposed CPU implementation, showing an “incoming” 16-bit instruction denoted `cccccccccccccccc`. The instruction bits are labeled `c`, since in the case of a C-instruction, the CPU logic treats them as control bits that are extracted from the instruction and routed to different chip-parts of the CPU. In particular, in this diagram, every `c` symbol entering a chip-part stands for some control bit, extracted from the instruction (in the case of the ALU, the “`c's`” input stands for the 6 control bits that instruct the ALU what to compute, and the “`c's`” output stands for its `zr` and `ng` outputs). Taken together, the distributed behaviors that these control bits effect throughout the CPU architecture end up executing the instruction.

Instruction decoding

The 16-bit value of the CPU's instruction input represents either an *A*-instruction or a *C*-instruction. In order to figure out the semantics of this instruction, we can parse, or unpack it, into the following fields: “*ixxacccccddjjj*”. The *i*-bit (also known as *opcode*) codes the instruction *type*, which is either 0 for an *A*-instruction or 1 for a *C*-instruction. In case of an *A*-instruction, the entire instruction represent the 16-bit value of the constant that should be loaded into the A register. In case of a *C*-instruction, the *a*- and *c*-bits code the *comp* part of the instruction, while the *d*- and *j*-bits code the *dest* and *jump* parts of the instruction, respectively (the *x*-bits are not used, and can be ignored).

Instruction Execution

The decoded fields of the instruction (*i*-, *a*-, *c*-, *d*-, and *j*-bits) are routed simultaneously to various parts of the CPU architecture, where they cause different chip-parts to do what they are supposed to do in order to execute either the *A*- or the *C*-instruction, as mandated by the Hack machine language specification. In the case of a *C*-instruction, the single *a*-bit determines whether the ALU will operate on the A register input or on the M input, and the six *c*-bits determine which function the ALU will compute. The three *d*-bits are used to determine which registers should “accept” the ALU resulting output, and the three *j*-bits are used to for branching control, as we now turn to describe.

Instruction Fetching

As a side effect of executing the current instruction, the CPU must determine, and emit, the address of the instruction that should be fetched and executed next. The key element in this sub-task is the *Program Counter*—a CPU chip-part whose role is to always store the address of the next instruction. Later in the chapter we'll describe how we connect the *pc* output of the CPU into the address input of the instruction memory; this connection causes the instruction

memory to always emit the instruction that ought to be fetched and executed next. This output is connected to the instruction input of the CPU, closing the fetch-execute cycle.

According to the Hack computer specification, the current program is stored in the instruction memory, starting at address 0. Hence, if we wish to start (or restart) a program's execution, we should reset the Program Counter to 0. That's why in diagram 5.8 the reset input of the CPU is fed directly into the reset input of the PC chip. If we'll assert this bit, we'll effect $PC=0$, causing the computer to fetch and execute the first instruction in the program. What should we do next? Normally, we'd like to execute the next instruction in the program. Therefore, the default operation of the Program Counter is $PC++$.

But what if the instruction dictates to effect a "jump n " operation, where n is the address of an instruction located anywhere in the program? According to the Hack language specification, a "jump n " operation is realized using a sequence of two instructions. First, we issue the *A*-instruction @ n , which sets the A register to n ; next, we issue a *C*-instruction that includes a jump directive. According to the language specification, execution always branches to the instruction that the A register points at. Thus, when implementing the CPU, one of our challenges is to come up with a logic gate architecture that realizes the following behavior: if *jump* then $PC = A$ else $PC++$. The value of the Boolean expression *jump* depends on the instruction's j-bits and on the ALU output.

How to implement this logic? The answer is hinted by diagram 5.8. Note that the output of the A register feeds into the input of the PC register. Recall that the latter chip has a load-bit that enables it to accept a new input value. Thus, if we'll assert this load-bit, we'll cause the architecture to effect the operation $PC=A$ rather than the default operation $PC++$. We should do this only if we have to realize a jump. Now, the question of whether or not a jump should be realized is answered by two signals: (i) the j-bits of the current instruction, specifying the jump

condition, and (ii) the ALU output-bits `zr` and `ng`, which can be used to determine if the specified condition is satisfied, or not.

We'll stop here, lest we rob readers the pleasure of discovering the missing details and completing the CPU implementation on their own.

5.3.2 Memory

The Hack Memory chip is essentially an amalgamation of three lower-level chips: RAM16K, Screen, and Keyboard. Yet this modularity is strictly implicit: users of the Memory chip, like Hack programmers or programmers who write compilers that generate Hack code, see a *single address space*, spanning from address 0 to address 24576 (`0x0000` to `0x6000` in hexa).

The implementation of the Memory chip (as shown in diagram 5.6) should realize this continuum effect. For example, if the address input of the Memory chip happens to be 16384, the chip logic should end up accessing address 0 in the Screen chip, and so on. This can be done using similar techniques to those used in chapter 3 to integrate small RAM units into larger ones.

5.3.3 Computer

We have reached the end of our hardware journey. The topmost Computer chip can be realized using three previously built chip-parts: a CPU, a data Memory, and an instruction memory named ROM32K. Diagram 5.9 gives the details.

 


Diagram 5.9: Proposed implementation of the platform's topmost chip, Computer.

5.4 Project

Objective: Build the Hack computer platform, culminating in the topmost Computer chip.

Resources: The only resources that you need for completing this project are the hardware simulator supplied with the book and the test materials described here. The computer platform should be written in HDL and tested using the hardware simulator.

Contract: Build a hardware platform capable of executing programs written in the Hack machine language specified in chapter 4. Demonstrate the platform's operations by having your Computer chip run the three programs described below.

Test Programs: A natural way to test the overall Computer chip implementation is to have it execute some sample programs written in the Hack machine language. In order to run such a

test, one can write a test script that loads the Computer chip into the hardware simulator, loads a program from an external text file into its ROM chip, and then runs the clock enough cycles to execute the program. We supply the following test programs (as well as all the relevant test scripts and compare files):

- `Add.hack`: Adds the two constants 2 and 3 and writes the result in `RAM[0]`.
- `Max.hack`: Computes the maximum of `RAM[0]` and `RAM[1]` and writes the result in `RAM[2]`.
- `Rect.hack`: Draws on the screen a rectangle of `RAM[0]` rows of 16 pixels each.

Before testing your Computer chip on any one of the above programs, read the test script associated with the program and be sure to understand the instructions given to the simulator. If needed, consult Appendix B.

Steps: Implement the hardware platform in the following order:

Memory: Composed from three chips: `RAM16K`, `Screen`, and `Keyboard`. The `Screen` and the `Keyboard` are available as built-in chips and there is no need to build them. Although the `RAM16K` chip was built in project 3, we recommend using its built-in version, as it provides a debugging-friendly GUI.

CPU: The central processing unit can be built according to the proposed implementation given in figure 5.8, using the `ALU` and `Register` chips built in chapters 2 and 3, respectively. We recommend using the built-in versions of these chips, in particular `ARegister` and `DRegister`. These chips have exactly the same functionality of the `Register` chip specified in chapter 3, plus GUI side effects.

In the course of implementing the CPU, you may be tempted to specify and build some internal chips of your own. Be advised that there is no need to do so; The Hack CPU can be implemented elegantly and efficiently using only the chip-parts that appear in diagram 5.8, plus some elementary logic gates built in project 1.

Instruction Memory: Use the built-in ROM32K chip.

Computer: Build the topmost Computer chip using the three chip-parts shown in diagram 5.9.

The Hardware Simulator: All the chips in this project (including the topmost Computer chip) can be implemented and tested using the supplied hardware simulator. Figure 5.10 is a screen shot of testing the Rect.hack program on a Computer chip implementation.

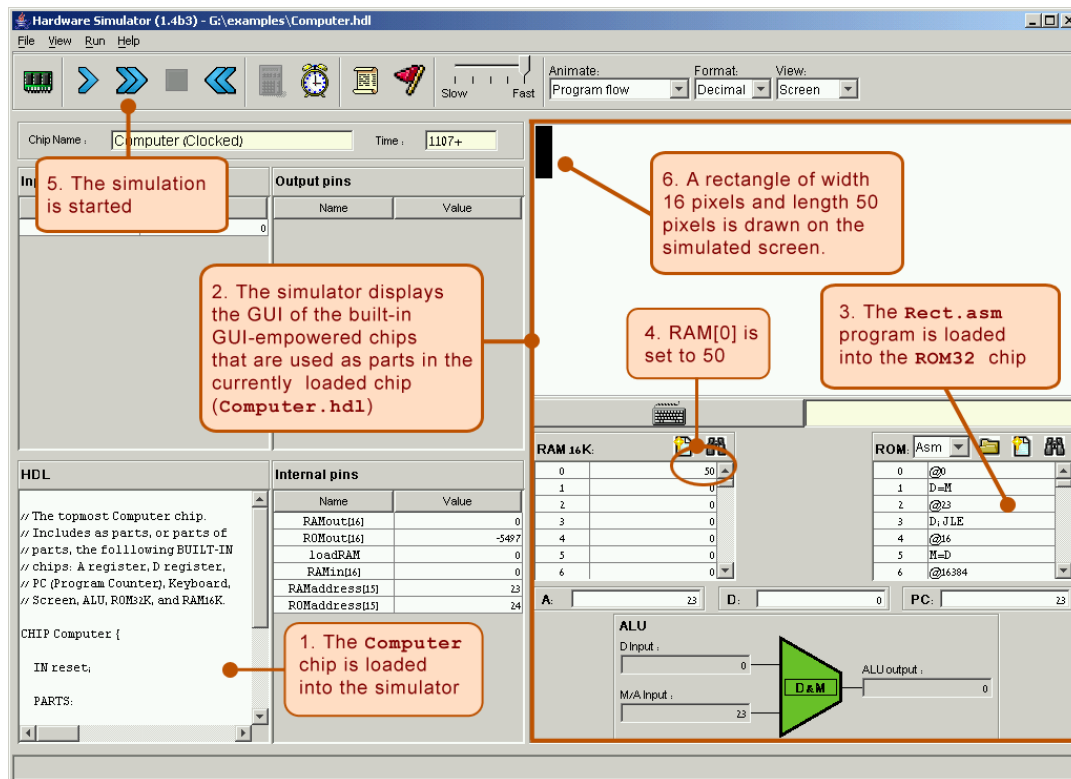


Diagram 5.10: Testing the Computer chip on the supplied hardware simulator. The Rect program draws a rectangle of RAM[0] rows of 16 pixels each, all black, at the top-left of the screen. Note that the program is error-free. Therefore, if it does not operate as expected, it means that the hardware platform on which it is running (Computer.hdl and/or, possibly, some of its chip-parts) is buggy.

5.5 Perspective

Following the general spirit of the book, the architecture of the Hack computer is rather minimal. Typical computer platforms have more registers, more data types, more powerful ALUs, and richer instruction sets. However, these differences are mainly quantitative. From a qualitative standpoint, Hack is quite similar to most digital computers, as they all follow the same conceptual paradigm: the von Neumann architecture.

In terms of function, computer systems can be classified into two categories: *general-purpose computers*, designed to easily switch from executing one program to another, and *dedicated computers*, usually embedded in other systems like cell phones, game consoles, digital cameras, weapon systems, factory equipment, and so on. For any particular application, a single program is burned into the dedicated computer's ROM, and is the only one that can be executed (in game consoles, for example, the game software resides in an external cartridge that is simply a replaceable ROM module encased in some fancy package). Aside from this difference, general-purpose and dedicated computers share the same architectural ideas: stored programs, fetch-decode-execute logic, CPU, registers, program counter, and so on.

Unlike Hack, most general-purpose computers use a single address space for storing both data and instructions. In such architectures, the instruction address as well as the optional data address specified by the instruction must be fed into the same destination: the single address input of the shared address space. Clearly, this cannot be done at the same time. The standard solution is to base the computer implementation on a two-cycle logic. During the *fetch cycle*, the instruction address is fed to the address input of the memory, causing it to immediately emit the current instruction, which is then stored in an *instruction register*. In the subsequent *execute cycle*, the instruction is decoded, and the optional data address inferred from it is fed to the memory's address input, allowing the instruction to manipulate the selected memory location. In contrast, the Hack architecture is unique in that it partitions the address

space into two separate parts, allowing a single-cycle fetch-execute logic. The price of this simpler hardware design is that programs cannot be changed dynamically.

In terms of I/O, the Hack keyboard and screen are rather spartan. General-purpose computers are typically connected to multiple I/O devices like printers, disks, network connections, and so on. Also, typical screens are obviously much more powerful than the Hack screen, featuring more pixels, many brightness levels in each pixel, and colors. Still, the basic principle that each pixel is controlled by a memory-resident binary value is maintained: instead of a single bit controlling the pixel's black or white color, several bits are devoted to control the level of brightness of each of the three primary colors that, together, produce the pixel's ultimate color. Likewise, the memory mapping of the Hack screen is simplistic. Instead of mapping pixels directly into bits of memory, most modern computers allow the CPU to send high-level graphic instructions to a *graphics card* that controls the screen. This way, the CPU is relieved from the tedium of drawing figures like circles and polygons directly—the graphics card takes care of this task using its own embedded chip-set.

Finally, it should be stressed that most of the effort and creativity in designing computer hardware is invested in achieving better performance. Thus, hardware architecture courses and textbooks typically evolve around such issues as implementing memory hierarchies (cache), better access to I/O devices, pipelining, parallelism, instruction prefetching, and other optimization techniques that were sidestepped in this chapter.

Historically, attempts to enhance the processor's performance have led to two main schools of hardware design. Advocates of the *Complex Instruction Set Computing* (CISC) approach argue for achieving better performance by providing rich and elaborate instruction sets. Conversely, the *Reduced Instruction Set Computing* (RISC) camp uses simpler instruction sets in order to promote as fast a hardware implementation as possible. The Hack computer

does not enter this debate, featuring neither a strong instruction set nor special hardware acceleration techniques.